

## 1 Review: Single-Cycle Datapath

1.1 True or False? The single cycle datapath uses the outputs of all hardware units for each instruction.

False. All units are active in each cycle, but their output may be ignored (gated) by control signals.

1.2 True or False? It is possible to execute the stages of the single-cycle datapath in parallel to speed up execution of a single instruction.

False. Each stage depends on the value produced by the stage before it (e.g., instruction decode depends on the instruction fetched). We *can* execute the stages in parallel if we insert registers to pipeline the stages.

1.3 Fill out the following table with the control signals for each instruction based on the single-cycle datapath on the last page.

- If the value of the signal does not affect the execution of an instruction, use the \* (don't care) symbol to indicate this.
- For ALUSel, write the ALU operation (**add**, **or**, **sll**, ...)

	BrEq	BrLT	PC-Sel	Imm-Sel	BrUn	ASel	BSel	ALUSel	MemRW	Reg-WEn	WB-Sel
xor	*	*	0	*	*	0 (Reg)	0 (Reg)	xor	0	1	1 (ALU)
lb	*	*	0	I	*	0 (Reg)	1 (Imm)	add	0	1	0 (MEM)
jalr	*	*	1 (ALU)	I	*	0 (rs1)	1 (Imm)	add	0	1	2 (PC + 4)

For this exercise, the times for each circuit element is given as follows:

**Register clk-to-q** 30 ps    **Branch comp.** 75 ps    **DMEM write setup** 200 ps  
**Register setup** 20 ps    **ALU** 200 ps    **Memory read** 250 ps  
**Register hold** 10 ps    **Imm. Gen.** 15 ps    **Mux** 25 ps  
**RegFile read** 100 ps    **RegFile setup** 20 ps

1.4 How long does it take to execute each instruction? Refer to the single-cycle datapath on the last page of the worksheet.

(a) ori

$$\begin{aligned}
 \text{ori} &= \text{clk-to-Q} + \text{IMEM Read} + \text{Regfile Read} + \text{Mux(ASel)} + \text{ALU} + \text{Mux(PCSel)} + \text{PCSetup} \\
 &= 30 \text{ ps} + 250 \text{ ps} + 100 \text{ ps} + 25 \text{ ps} + 200 \text{ ps} + 25 \text{ ps} + 20 \text{ ps} \\
 &= 650 \text{ ps}
 \end{aligned}$$

Note that we take the maximum of the path from IMEM->Regfile->Mux->ALU and IMEM->ImmGen->Mux->ALU. With this hardware configuration, the longest path is through the Register file + ASel Mux.

(b) lh

$$\begin{aligned}
 \text{lh} &= \text{clk-to-Q} + \text{IMEM Read} + \max(\text{RegFile Read} + \text{Mux(ASel)}, \text{ImmGen} + \text{Mux(BSel)}) \\
 &\quad + \text{ALU} + \text{Mem-Read} + \text{Mux(WBSel)} + \text{RegFileSetup} \\
 &= 30 \text{ ps} + 250 \text{ ps} + 60 \text{ ps} + \max(100 \text{ ps} + 25 \text{ ps}, 15 \text{ ps} + 20 \text{ ps}) + 200 \text{ ps} + 250 \text{ ps} + 25 \text{ ps} + 20 \text{ ps} \\
 &= 30 \text{ ps} + 250 \text{ ps} + 60 \text{ ps} + 125 \text{ ps} + 200 \text{ ps} + 250 \text{ ps} + 25 \text{ ps} + 20 \text{ ps} \\
 &= 900 \text{ ps}
 \end{aligned}$$

1.5 Which instruction(s) are responsible for the critical path?

Load instructions use all 5 datapath stages (lh calculated above takes 900 ps)

1.6 Why is the single-cycle datapath inefficient?

At any given time, most of the parts of the single cycle datapath are not being used. Even though not every instruction exercises the critical path, the datapath can only be clocked as fast as the slowest instruction.

## 2 Performance Analysis

<b>Register clk-to-q</b> 30 ps	<b>Branch comp.</b> 75 ps	<b>DMEM write setup</b> 200 ps
<b>Register setup</b> 20 ps	<b>ALU</b> 200 ps	<b>Memory read</b> 250 ps
<b>Register hold</b> 10 ps	<b>Imm. Gen.</b> 15 ps	<b>Mux</b> 25 ps
<b>RegFile read</b> 100 ps	<b>RegFile setup</b> 20 ps	

Given above are sample delays and setup times for each of the datapath components and registers. In the questions below, use these in conjunction with the pipelined datapath on the last page to answer them.

2.1 What would be the fastest possible clock time for a **single cycle** datapath? Recall from last week's discussion that one instruction which exercises the critical path is **lw**.

(HINT:  $t_{\text{clk-cycle}} \geq t_{\text{clk-to-q}} + t_{\text{longest-combinational-path}} + t_{\text{setup}}$ )

$$\begin{aligned} t_{\text{clk}} &\geq t_{\text{PC clk-to-q}} + t_{\text{IMEM read}} + t_{\text{RF read}} + t_{\text{mux}} + t_{\text{ALU}} + t_{\text{DMEM read}} + t_{\text{mux}} + t_{\text{RF setup}} \\ &\geq 30 + 250 + 100 + 25 + 200 + 250 + 25 + 20 \\ &\geq 900 \text{ ps} \end{aligned}$$

Note that the delay in the immediate generator as well as the branch comparator are omitted because the immediate generator and branch comparison is done in parallel with the RegFile read and ALU computation respectively, the latter two taking much longer time.

2.2 What is the fastest possible clock time for a pipelined datapath?

$$\begin{aligned} \text{IF} &: t_{\text{PC clk-to-q}} + t_{\text{IMEM read}} + t_{\text{Reg setup}} = 30 + 250 + 20 = 300 \text{ ps} \\ \text{ID} &: t_{\text{Reg clk-to-q}} + t_{\text{RF read}} + t_{\text{Reg setup}} = 30 + 100 + 20 = 150 \text{ ps} \\ \text{EX} &: t_{\text{Reg clk-to-q}} + t_{\text{mux}} + t_{\text{ALU}} + t_{\text{Reg setup}} = 30 + 25 + 200 + 20 = 275 \text{ ps} \\ \text{MEM} &: t_{\text{Reg clk-to-q}} + t_{\text{DMEM read}} + t_{\text{Reg setup}} = 30 + 250 + 20 = 300 \text{ ps} \\ \text{WB} &: t_{\text{Reg clk-to-q}} + t_{\text{mux}} + t_{\text{RF setup}} = 30 + 25 + 20 = 75 \text{ ps} \\ t_{\text{clk}} &\geq \max(\text{IF}, \text{ID}, \text{EX}, \text{MEM}, \text{WB}) = 300 \text{ ps} \end{aligned}$$

The immediate generator and branch comparator delays are overshadowed by the longer delays of RegFile read and ALU.

2.3 What is the speedup from the single cycle datapath to the pipelined datapath? Why is the speedup less than 5x?

$\frac{900 \text{ ps}}{300 \text{ ps}} = 3x$  speedup. The speedup is less than 5 because:

- 1) the necessity of adding pipeline registers, which have clk-to-q and setup times
- 2) the need to set the clock to the *maximum* of the five stages.

Note: Hazards require additional logic to resolve which would result in an even smaller performance increase.

### 3 Solving Data Hazards

One of the costs of pipelining is that it introduces pipeline hazards. Hazards, generally, are issues with something in the CPU's instruction pipeline that could cause the next instruction to execute incorrectly. Recall that **data hazards** are caused by data dependencies between instructions. In CS 61C, where we always assume that instructions go through the processor in order, we see data hazards when an instruction reads a register before a previous instruction has finished writing to that register.

For all questions, assume no branch prediction or double-pumping (i.e. write-then-read in one cycle for RegFile).

**Forwarding**

Most data hazards can be resolved by forwarding, which is when the result of the EX or MEM stage is sent to the EX stage for a following instruction to use.

Side note: how is forwarding (EX to EX or MEM to EX) implemented in hardware? We add 2 wires: one from the beginning of the MEM stage for the output of the ALU and one from the beginning of the WB stage. Both of these wires will connect to the A/B muxes in the EX stage.

- 3.1 Look for data hazards in the code below, and figure out how forwarding could be used to solve them.

Instruction	C1	C2	C3	C4	C5	C6	C7
1. <code>addi t0, a0, -1</code>	IF	ID	EX	MEM	WB		
2. <code>and s2, t0, a0</code>		IF	ID	EX	MEM	WB	
3. <code>sltiu a0, t0, 5</code>			IF	ID	EX	MEM	WB

There are two data hazards, between instructions 1 and 2, and between instructions 1 and 3. The first could be resolved by forwarding the ALU output in the MEM stage to the beginning of the EX stage in C4, and the second could be resolved by forwarding the ALU output in the WB stage in C5 to the beginning of the EX stage in C5.

- 3.2 Imagine you are a hardware designer working on a CPU's forwarding control logic. How many instructions after the `addi` instruction could be affected by data hazards created by this `addi` instruction?

Three instructions. For example, with the `addi` instruction, any instruction that uses `t0` that has its ID stage in C3, C4, or C5 will not have the result of `addi`'s writeback in C5. If, however, we are allowed to assume double-pumping (write-then-read to registers), then it would only affect two instructions since the ID stage of instruction 4 would be allowed to line up with the WB stage of instruction 1.

**Stalls**

- 3.3 Identify the data hazards in the code below. One of them cannot be solved with forwarding—why? What can we do to solve this hazard?

Instruction	C1	C2	C3	C4	C5	C6	C7	C8
1. <code>addi s0, s0, 1</code>	IF	ID	EX	MEM	WB			
2. <code>addi t0, t0, 4</code>		IF	ID	EX	MEM	WB		
3. <code>lw t1, 0(t0)</code>			IF	ID	EX	MEM	WB	

Instruction	C1	C2	C3	C4	C5	C6	C7	C8
4. add t2, t1, x0				IF	ID	EX	MEM	WB

There are two data hazards in the code. The first hazard is between instructions 2 and 3, from t0, and the second is between instructions 3 and 4, from t1. The hazard between instructions 2 and 3 can be resolved with forwarding, but the hazard between instructions 3 and 4 cannot be resolved with forwarding. This is because even with forwarding, instruction 4 needs the result of instruction 3 at the beginning of C6, and it won't be ready until the end of C6.

We can fix this by stalling: insert a nop (no-operation) between instructions 3 and 4.

- 3.4 Say you are the compiler and can re-order instructions to minimize data hazards while guaranteeing the same output. How can you fix the code above?

Reorder the instructions 2-3-1-4, because instruction 1 has no dependencies.

### Control Hazards

Control hazards are caused by jump and branch instructions, because for all jumps and some branches, the next PC is not PC + 4, but the result of the ALU available after the EX stage. We could stall the pipeline for control hazards, but this decreases performance.

- 3.5 Identify the control hazards in the code below. How can we resolve them?

Instruction	C1	C2	C3	C4	C5	C6	C7	C8	C9
1. beq s0, s1, loop	IF	ID	EX	MEM	WB				
2. addi t0, t0, 4		IF	ID	EX	MEM	WB			
3. ori t1, t1, 7			IF	ID	EX	MEM	WB		
4. slli sp, sp, 2				IF	ID	EX	MEM	WB	
5. addi a0, t0 2					IF	ID	EX	MEM	WB

There are three control hazards in the code. The first hazard is between instructions 1 and 2 because `addi t0, t0, 4` may not get executed if the branch condition is true. The second hazard is between instructions 1 and 3 for the same reason as above and similarly between instructions 1 and 4. The branch condition and ALU outputs are available at the start of the MEM stage (look at the pipeline register placement!) in C4, so we have to stall for 3 cycles. There is no control hazard between instructions 1 and 5 because there is no need to stall instruction 5 if the branch is not taken.

We can fix the hazards by stalling: insert three NOPs (no-operation) after the first instruction.

3.6 Besides stalling, what can we do to resolve control hazards?

We can try to predict which way branches will go, and if this prediction is incorrect, flush the pipeline and continue with the correct instruction. No branch prediction will always incur 3 stalls, while branch prediction can save 3 stalls on a correct prediction.

## 4 Hazards Practice

Given the RISC-V code below and a 5-stage pipelined CPU with no forwarding, how many hazards would there be? What types are each hazard? Consider all possible hazards between all instructions.

How many stalls would there need to be in order to fix the data hazard(s) if the RegFile supports double-pumping (i.e. write-then-read)? What about the control hazard(s) if we use branch prediction with perfect accuracy?

Instruction	C1	C2	C3	C4	C5	C6	C7	C8	C9
(a) <code>sub t1, s0, s1</code>	IF	ID	EX	MEM	WB				
(b) <code>or s0, t0, t1</code>		IF	ID	EX	MEM	WB			
(c) <code>sw s1, 100(s0)</code>			IF	ID	EX	MEM	WB		
(d) <code>bgeu s0, s2, loop</code>				IF	ID	EX	MEM	WB	
(e) <code>add t2, x0, x0</code>					IF	ID	EX	MEM	WB

There are four hazards: between instructions 1 and 2 (data hazard from t1), instructions 2 and 3 (data hazard from s0), instructions 2 and 4 (from s0), and instructions 4 and 5 (a control hazard).


Assuming that we can read and write to the RegFile on the same cycle, two stalls are needed between instructions 1 and 2 (WB→ID), and two stalls are needed between instructions 2 and 3 (WB→ID). For the control hazard, if we predicted correctly, then no stalls are needed, but if we predicted incorrectly, then we need 3 stalls to flush the pipeline (MEM→1 cycle before IF). We don't need to stall for the hazard between 2 and 4 because stalling for instruction 3 already handles that.

Instruction	C1	C2	C3	C4	C5	C6	C7	C8	C9
1. sub t1, s0, s1	IF	ID	EX	MEM	WB				
nop		IF	X	X	X	X			
nop			IF	X	X	X	X		
2. or s0, t0, t1				IF	ID	EX	MEM	WB	
nop					IF	X	X	X	X
nop						IF	X	X	X
3. sw s1, 100(s0)							IF	ID	EX
4. bgeu s0, s2, loop								IF	ID
5. add t2, x0, x0									IF

Instruction	...	C10	C11	C12	C13	C14	C15	C16	C17
nop	...	X							
3. sw s1, 100(s0)	...	MEM	WB						
4. bgeu s0, s2, loop	...	EX	MEM	WB					
5. add t2, x0, x0	...	ID	EX	MEM	WB				

Note that NOP is a pseudoinstruction for `addi x0, x0, x0` and still goes through the ID-WB stages.

### Single-Cycle Datapath Diagram

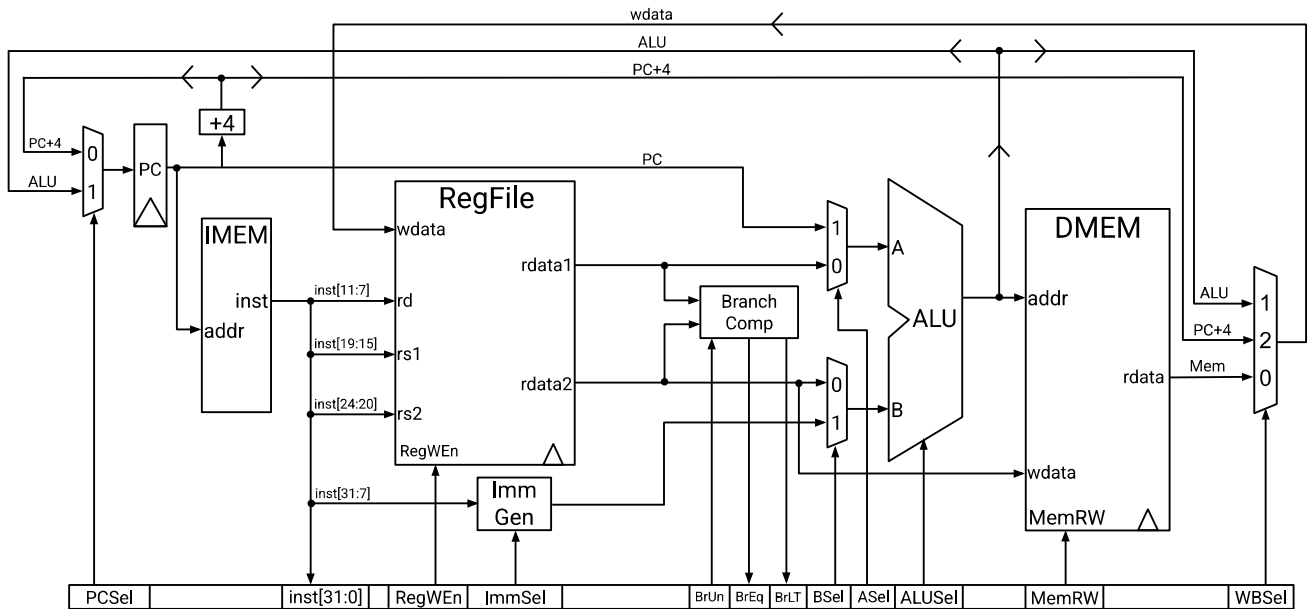

### 5-Stage Datapath Diagram

