

1 Pre-Check

This section is designed as a conceptual check for you to determine if you conceptually understand and have any misconceptions about this topic. Please answer true/false to the following questions, and include an explanation:

- 1.1 The single cycle datapath uses the outputs of all hardware units for each instruction.

- 1.2 It is possible to execute the stages of the single cycle datapath in parallel to speed up execution of a single instruction.

- 1.3 If the logic delay of reading from IMEM is reduced, then any (non-empty) program using the single cycle datapath will speed up.

- 1.4 Stores and loads are the only instructions that require input/output from DMEM.

- 1.5 It is possible to feed both the immediate generator's output and the value in rs2 to the ALU in a single instruction.

2 Single-Cycle CPU

2.1 For this worksheet, we will be working with the single-cycle CPU datapath provided the last page.

- (a) Explain what happens in each datapath stage, and which hardware units in the datapath are used.

IF Instruction Fetch

ID Instruction Decode

EX Execute

MEM Memory

WB Writeback

- (b) On the datapath on the last page of the worksheet, fill in each **round** box with the name of the datapath component, and each **square** box with the name of the control signal.

3 Timing the Datapath

3.1 Clocking Methodology

- A **state element** is an element connected to the clock (denoted by a triangle at the bottom). The **input signal** to each state element must stabilize before each **rising edge**.
- The **critical path** is the longest delay path between state elements in the circuit. The circuit cannot be clocked faster than this, since anything faster would mean that the correct value is not guaranteed to reach the state element in the allotted time. If we place registers in the critical path, we can shorten the period by **reducing the amount of logic between registers**.

For this exercise, the times for each circuit element is given as follows:

Clk-to-Q	RegFile Read	PC/RegFile Setup	Mux	Adder
5ns	35ns	20ns	15ns	20ns

ALU	Branch Comp	Imm Gen	MEM Read	DMEM Setup
100ns	50ns	45ns	300ns	200ns

- (a) Mark an **X** for the stages used by each instruction:

	IF	ID	EX	MEM	WB	
add						
ori						
lw						
sw						
beq						
jal						

- (b) How long does it take to execute each instruction? Ignore the length of a clock cycle based off of the critical path, and assume that the setup times to the RegFile and the PC are the same.

1. jal

2. lw

3. sw

- (c) Which instruction(s) are responsible for the critical path?

- (d) What is the highest clock frequency for this single cycle datapath?

- (e) Why is the single cycle datapath inefficient?

- (f) How can you improve its performance? What is the purpose of pipelining?

